

# Digital Logic Structures

# Electrons


- Are tiny
- Are negatively charged
- Hurt
- Are the basis for our modern society

# Circuits

- A circuit is a path which allows electrons to flow.
- A generator or battery provides the push to the electrons known as Voltage.
- Pushing the electrons doesn't mean they will move.
- Electrons can only move if they have somewhere to move.
- Think of pushing a line of people against a closed door. The people won't move no matter how hard you push.
- Open the door and they all fall down.
- When electrons move that is called Current.

 
# Magnets Move Electrons

- The magnet, the electron, and the wire.



 
# A wire is FULL of electrons.

- Will this work? This is a complete circuit.
- Think of it like a bicycle chain.
- The moving magnet provides pressure or voltage.



 
# Open Circuit.

- Electrons can't leave the wire (normally).
- The pressure is still being applied (moving magnet).
- Voltage is present even if current is not flowing.



 
# The Switch

- If the pressure (voltage) is there ...
- closing the switch lets electrons flow (current).


 
# Source and Ground


- One side supplies electrons =  $2.9V = 1$
- One side provides path back = ground =  $0$





 
# Why Ground?

- One side (the return side) is sometimes connected to the actual ground.
- The electrical system in your home is **ALWAYS** connected to earth this way.




 
# Transistors

- A transistor is like an electronic switch.
- Metal Oxide Semiconductor (MOS)
- The GATE is the control.
- 1 = on = closed = conducting
- 0 = off = open = not conducting



  
# Light Circuit with Transistor

- 1 on Gate turns transistor "on".
- Transistor "on" means a complete path.
- A complete path means current flow.
- Current flow means light.



# Electrons Move Easily

- The electrons here move TOO easily.

 

- If there is nothing to slow the electrons down the material quickly overheats and will probably melt.
- You MUST always have some sort of resistance to current flow to prevent this


# Important Points

- A transistor is a switch that can be considered open or closed.
- Voltage levels, not current, represent 1s and 0s.
- 1 is usually some positive voltage and 0 is a connection to ground or zero voltage.
- Voltage is present without current flow.
- You must always have some resistance in a circuit to prevent excessive heat.


# n-type or p-type

- n-type requires 1 to conduct
- p-type requires 0 to conduct

n-type

 


p-type

 

# Building Circuits


| in | out |
|----|-----|
| 0  |     |
| 1  |     |

 

We are trying to either connect voltage (1) or ground (0) to the output.

# Building Circuits


| in | out |
|----|-----|
| 0  | 1   |
| 1  |     |

 




# Building Circuits

| in | out |
|----|-----|
| 0  | 1   |
| 1  |     |

 

# Building Circuits


| in | out |
|----|-----|
| 0  | 1   |
| 1  | 0   |

 

# CMOS Inverter


Complementary because it has both n-type and p-type

| in | out |
|----|-----|
| 0  | 1   |
| 1  | 0   |

 


# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 | ? |
| 0 | 1 |   |
| 1 | 0 |   |
| 1 | 1 |   |

 


# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | ? |
| 1 | 0 | ? |
| 1 | 1 |   |

 

# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | ? |

 


These circuits are designed so that either 1 or 0 is ALWAYS connected to the output and so that 1 and 0 are never connected at the same time.

# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


So what is it?

 

# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 |   |
| 0 | 1 |   |
| 1 | 0 |   |
| 1 | 1 |   |


What is this?

 



# Fill in the truth table


| A | B | C |
|---|---|---|
| 0 | 0 |   |
| 0 | 1 | ? |
| 1 | 0 |   |
| 1 | 1 |   |

 

# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 |   |
| 0 | 1 | 1 |
| 1 | 0 |   |
| 1 | 1 |   |


What is this gate?

 

# Fill in the truth table

| A | B | C |
|---|---|---|
| 0 | 0 |   |
| 0 | 1 | 1 |
| 1 | 0 |   |
| 1 | 1 |   |


What is this gate?

 


# Fill in the truth table

| A | B | C | D |
|---|---|---|---|
| 0 | 0 |   |   |
| 0 | 1 |   |   |
| 1 | 0 |   |   |
| 1 | 1 |   |   |

What is this?

 

 

# And Gate

- And
  - The book uses the word ***and*** as the symbol
  - Logic uses  $\wedge$
  - Other digital sources use  $*$  (as in multiplication)
  - Examples:


A and B

$A \wedge B$

$A * B$

$AB$


- Electronic Symbol

 

| Truth Table |   |         |
|-------------|---|---------|
| A           | B | A and B |
| 0           | 0 | 0       |
| 0           | 1 | 0       |
| 1           | 0 | 0       |
| 1           | 1 | 1       |
 
# Or Gate

- Or
  - The book uses the word **or** as the symbol
  - Logic uses  $\vee$
  - Other digital sources use  $+$  (as in addition)
  - Examples
    - A or B       $A \vee B$        $A+B$
  - Electronic Symbol



| Truth Table |   |        |
|-------------|---|--------|
| A           | B | A or B |
| 0           | 0 | 0      |
| 0           | 1 | 1      |
| 1           | 0 | 1      |
| 1           | 1 | 1      |

# Inverter Gate


- Inverter

- The book uses the word ***not***
- Logic uses  $\neg$
- Other digital sources use an over line or ' (apostrophe)

- Examples

- not A       $A'$        $\bar{A}$

- Electronic Symbol

 

| Truth Table |       |
|-------------|-------|
| A           | not A |
| 0           | 1     |
| 1           | 0     |



# Nand Gate

- Nand

- Combination of "**not gate**" and "**and gate**"


- Examples (note that most require parenthesis):

not(A and B)       $\neg (A \wedge B)$        $(A * B)'$        $\overline{AB}$

- Note that these **ARE NOT** equivalent to the following

- not A and B      not A and not B       $\bar{A}\bar{B}$

- Electronic Symbol

 

| Truth Table |   |         |              |
|-------------|---|---------|--------------|
| A           | B | A and B | Not(A and B) |
| 0           | 0 | 0       | 1            |
| 0           | 1 | 0       | 1            |
| 1           | 0 | 0       | 1            |
| 1           | 1 | 1       | 0            |

# Nor Gate

- Nor

- Combination of "**not gate**" and "**or gate**"

- Examples (note that most require parenthesis):


$$\text{not}(A \text{ or } B) \qquad \neg (A \vee B) \qquad (A+B)'$$

$$\overline{A + B}$$

- Note that these **ARE NOT** equivalent to the following

- not A or B  $\qquad \qquad \qquad$  not A or not B  $\qquad \qquad \qquad$   $\bar{A} + \bar{B}$

- Electronic Symbol

 

| Truth Table |   |        |             |
|-------------|---|--------|-------------|
| A           | B | A or B | Not(A or B) |
| 0           | 0 | 0      | 1           |
| 0           | 1 | 1      | 0           |
| 1           | 0 | 1      | 0           |
| 1           | 1 | 1      | 0           |

# XOR - XNOR



| A | B | $A \wedge B$ |
|---|---|--------------|
| 0 | 0 | 0            |
| 0 | 1 | 1            |
| 1 | 0 | 1            |
| 1 | 1 | 0            |

| A | B | $(A \wedge B)'$ |
|---|---|-----------------|
| 0 | 0 | 1               |
| 0 | 1 | 0               |
| 1 | 0 | 0               |
| 1 | 1 | 1               |

- Exclusive OR (XOR) means A or B but not both.

$$A \oplus B = \bar{A}B + A\bar{B}$$

# N-Input Gates


- The gates shown with two inputs can have multiple input versions.
- The internals are more complicated but the result is the same.
- **And** gates will have an output of 0 if any of the inputs are 0.
- **Or** gates will have an output of 1 if any of the inputs are 1.

Three input examples:

And



Or

 

# DeMorgan's Laws

- You can use DeMorgan's Law to say the same thing in a different way.

- DeMorgan

not ( p or q ) is the same as not p and not q

not ( p and q ) is the same as not p or not q

- A phrase with a negation can be rewritten using DeMorgan

I do not speak either Spanish or German


I do not speak Spanish and I do not speak German

I do not drink and drive


I do not drink or I do not drive
 
# DeMorgan Version of Gates

- And:  $A \text{ and } B = \overline{\overline{A \text{ and } B}} = \overline{\overline{A} \text{ or } \overline{B}}$



 - Or:  $A \text{ or } B = \overline{\overline{A \text{ or } B}} = \overline{\overline{A} \text{ and } \overline{B}}$




# Combination Circuits

- Bigger circuits using gates to accomplish a specific task.
- Often it isn't important to see the internal workings as long as you know what they are and how they work.
  - Decoder
  - Multiplexor
  - Adder
  - Counter
 
# 2 to 4 Decoder


- Select a specific output pattern for each input pattern
- Typically a single output is 1 for a given input but others are possible (7 segment decoder).
- Think of it as decoding a binary number.
- This is a 2x4 decoder. Other sizes are common.





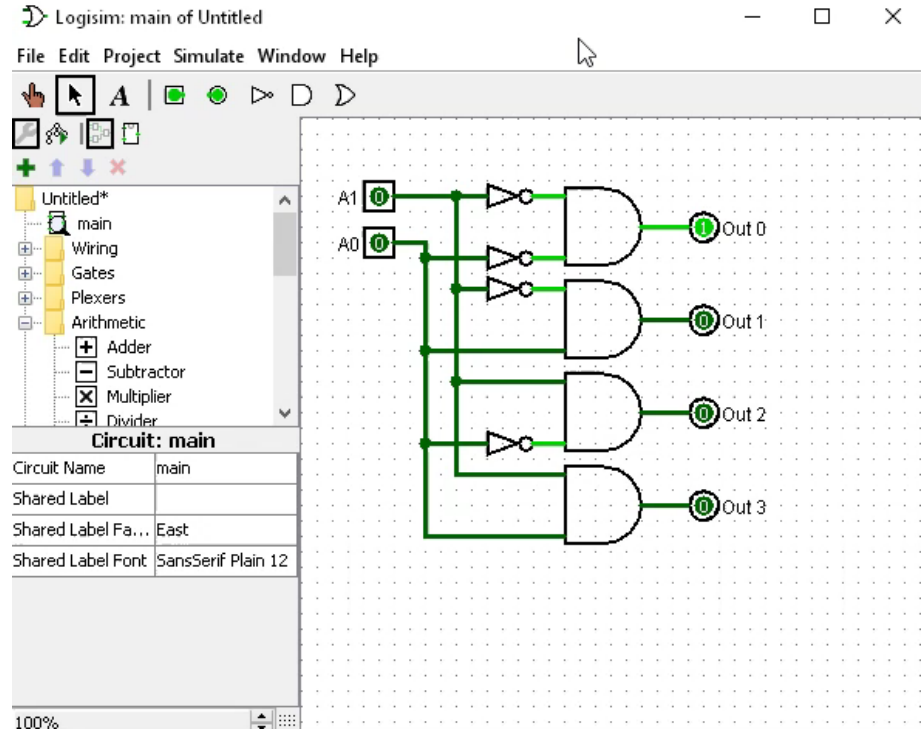
# Logisim

- Digital Logic Simulator
- Written in Java
- Works on any OS
- 4-bit Decoder



 
# 3 to 8 Decoder Block

- Could you draw the internals?
- Why 8 output lines?
- What would require 16 output lines?
- Assume 5 on input, what would the output be? What about 7?
- Build a 3 to 8 decoder in Logisim tonight.


 
# Multiplexer

- A multiplexer (or mux) is a digital selector.
- A multiplexer chooses one of several inputs to appear on an output.
- More complex multiplexers consist of multiple single multiplexers working together.



# Multiplexer

- S is the select bit (or bits).
- A and B are inputs.
- The value of A or B will appear on the output according to the value on S.

A=0, B=0, S=0, O=\_\_\_\_\_


A=0, B=1, S=0, O=\_\_\_\_\_

A=0, B=1, S=1, O=\_\_\_\_\_

A=1, B=0, S=0, O=\_\_\_\_\_


A=1, B=0, S=1, O=\_\_\_\_\_

A=1, B=1, S=1, O=\_\_\_\_\_

 

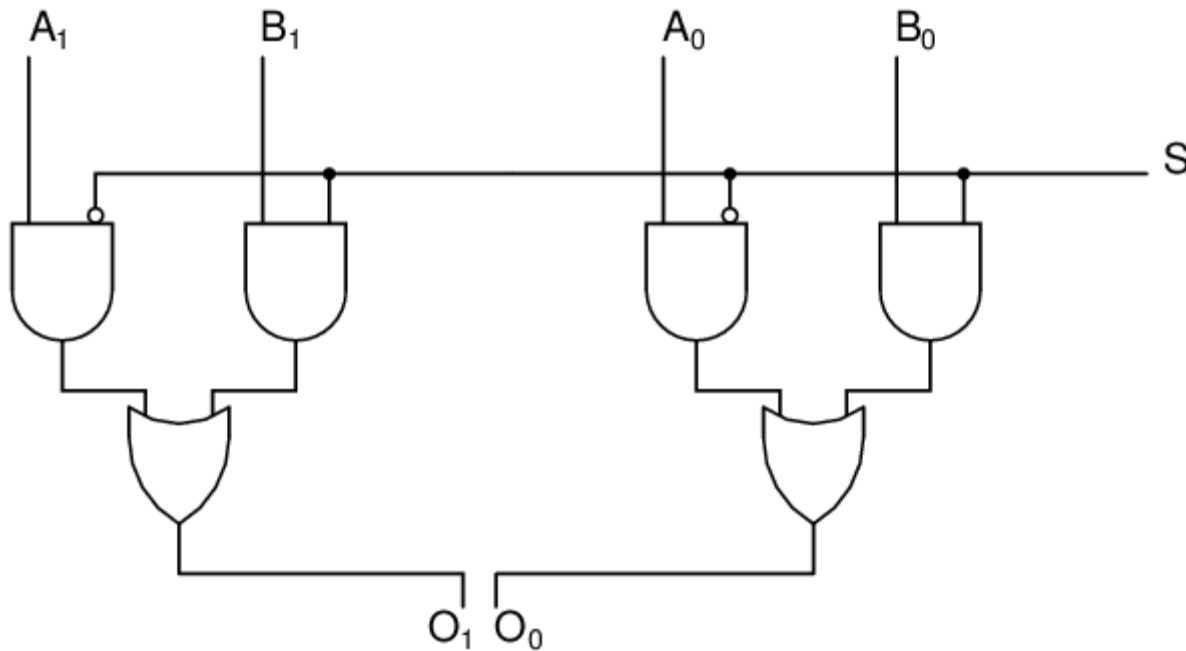
# More Complex Mux 4x2

- $A = 3, B = 2, S = 0$ : What is  $O$ ?
- $A = 1, B = 3, S = 1$ : What is  $O$ ?





# Another Complex Mux 4x1


 


# 4x1 vs 4x2

- Notice the difference

  


# 2x1 Block Diagram of a Mux

  




# 4x2 Block Diagram of a Mux

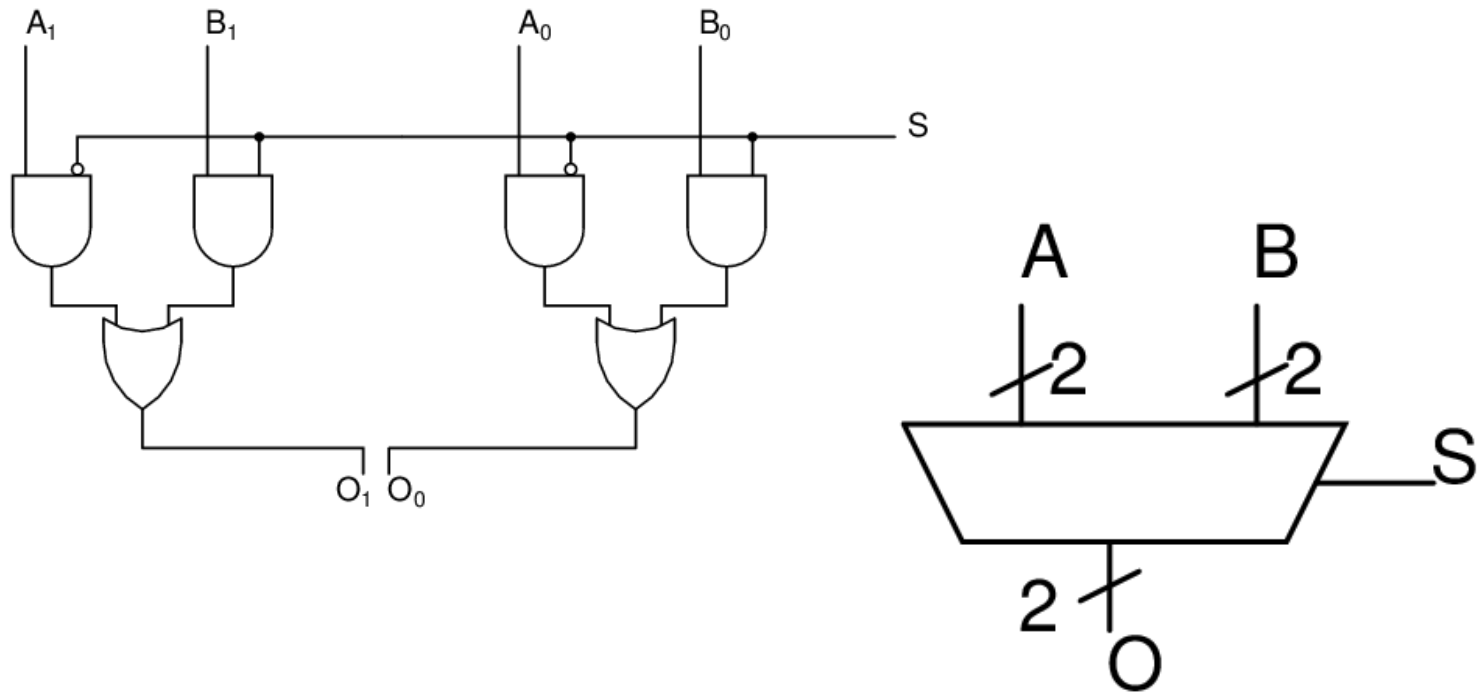

# 4x1 Block Diagram

 


**Homework:**

**Build a 16x4 Multiplexer in Logisim**

 
# Decoder as a Universal Circuit

- What is the output when  $A=0$ ,  $B=0$ , and  $C=0$ ?


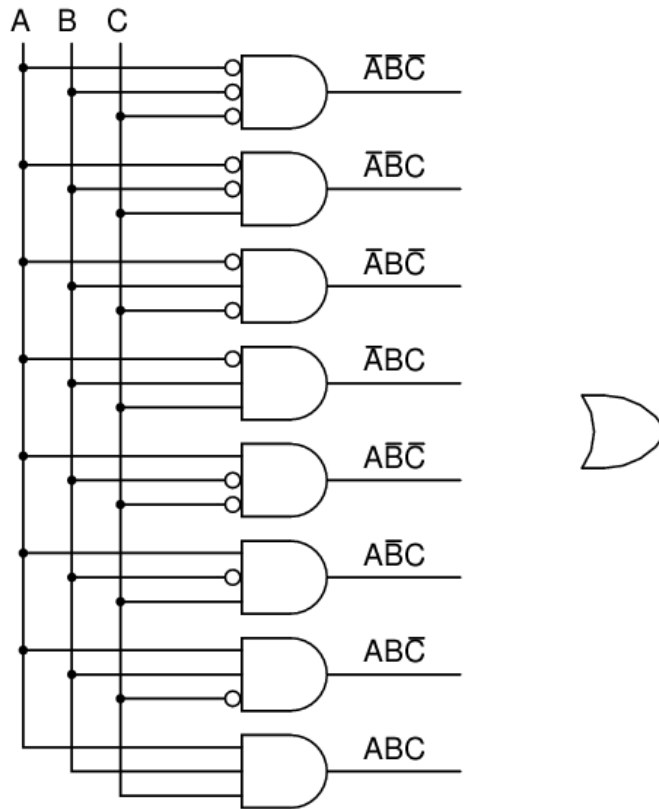
# Decoder as a Universal Circuit

- $f(A, B, C) = \bar{A}BC + \bar{A}\bar{B}C + ABC$



# Adding in Binary

Add A + B

|       |   |   |   |   |         |
|-------|---|---|---|---|---------|
|       | 1 | 1 | 1 | 0 | <-Carry |
|       | 0 | 1 | 1 | 1 | A=7     |
| +     | 0 | 0 | 1 | 1 | B=3     |
| <hr/> |   |   |   |   |         |
|       | 1 | 0 | 1 | 0 | (10)    |

What is required to add one column?

One bit from A, One bit from B, and a carry in.

What is the output?




Sum and Carry out.

# Truth table for adding one bit.


| Cin | Bit From A | Bit from B | Sum | Cout |
|-----|------------|------------|-----|------|
| 0   | 0          | 0          |     |      |
| 0   | 0          | 1          |     |      |
| 0   | 1          | 0          |     |      |
| 0   | 1          | 1          |     |      |
| 1   | 0          | 0          |     |      |
| 1   | 0          | 1          |     |      |
| 1   | 1          | 0          |     |      |
| 1   | 1          | 1          |     |      |

# Create the circuit

| $C_{in}$ | A | B | Sum | $C_{out}$ |
|----------|---|---|-----|-----------|
| 0        | 0 | 0 | 0   | 0         |
| 0        | 0 | 1 | 1   | 0         |
| 0        | 1 | 0 | 1   | 0         |
| 0        | 1 | 1 | 0   | 1         |
| 1        | 0 | 0 | 1   | 0         |
| 1        | 0 | 1 | 0   | 1         |
| 1        | 1 | 0 | 0   | 1         |
| 1        | 1 | 1 | 1   | 1         |

   



# Adder

 



  
# Adder Block Diagram


By creating a circuit for a single bit, it makes it easier to add more bits by simply duplicating the adder circuit for each bit.



# 4 bit adder

 

| Cin | B1 | B2 | Sum | Cout |
|-----|----|----|-----|------|
| 0   | 0  | 0  | 0   | 0    |
| 0   | 0  | 1  | 1   | 0    |
| 0   | 1  | 0  | 1   | 0    |
| 0   | 1  | 1  | 0   | 1    |
| 1   | 0  | 0  | 1   | 0    |
| 1   | 0  | 1  | 0   | 1    |
| 1   | 1  | 0  | 0   | 1    |
| 1   | 1  | 1  | 1   | 1    |

 

**Homework:**  
**Build a 4-bit Adder in Logisim**


# Storing 1s and 0s

- So far 1s and 0s have just appeared on inputs without explanation about where they come from.
- For a computer to add it needs an adder circuit, but the inputs must be stored somewhere on the computer also.
- The result, also, must get stored somewhere for it to be useful.
- We store these bits in a circuit called a latch.

# R-S Latch


NAND TRUTH TABLE

| A | B | $\overline{AB}$ |
|---|---|-----------------|
| 0 | 0 | 1               |
| 0 | 1 | 1               |
| 1 | 0 | 1               |
| 1 | 1 | 0               |

 

# R-S Latch

| R | S | Q         |
|---|---|-----------|
| 1 | 1 | No Change |
| 1 | 0 | 1         |
| 0 | 1 | 0         |
| 0 | 0 | Unused    |

 

1 on S and R means Q doesn't change.

0 on S means **set** Q to 1


0 on R means **reset** Q to 0

Do not put 0 on S and R at same time.

# The Gated D Latch


- A modified R-S latch.
  - A single input (D)
  - A write enable circuit (WE)
- A gate circuit directs inputs to R and S.

| D | WE | Q         |
|---|----|-----------|
| 0 | 0  | No Change |
| 0 | 1  | 0         |
| 1 | 0  | No Change |
| 1 | 1  | 1         |

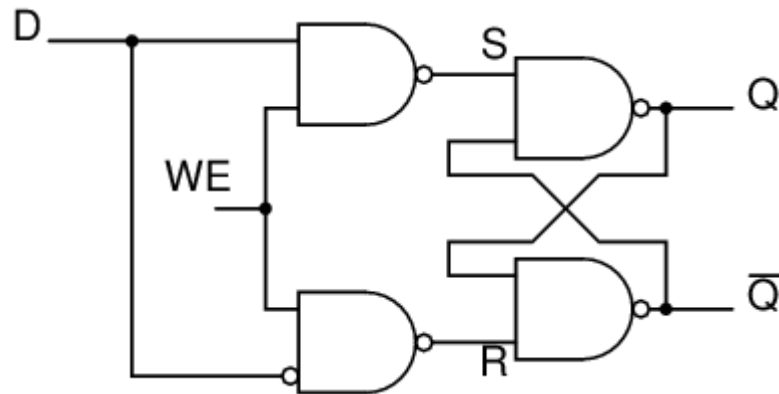
 
# Storing More than One Bit

- How could four bits be stored? Use four D latches working together.
- The device for storing multiple bits as a unit is called a **REGISTER**.
- Bigger numbers simply use more latches.
- 64 bit microprocessors use 64 latches for registers.



# Register Annotation

- The bits are labeled with subscripts from low order to high order which is typically right to left.
- The instruction register (IR) is a 16 bit register

| IR <sub>15</sub> | IR <sub>14</sub> | IR <sub>13</sub> | IR <sub>12</sub> | IR <sub>11</sub> | IR <sub>10</sub> | IR <sub>9</sub> | IR <sub>8</sub> | IR <sub>7</sub> | IR <sub>6</sub> | IR <sub>5</sub> | IR <sub>4</sub> | IR <sub>3</sub> | IR <sub>2</sub> | IR <sub>1</sub> | IR <sub>0</sub> |
|------------------|------------------|------------------|------------------|------------------|------------------|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|-----------------|
| 1                | 0                | 0                | 1                | 0                | 1                | 0               | 0               | 0               | 1               | 1               | 1               | 0               | 1               | 1               | 0               |

- We can refer to ranges of bits using brackets

IR[15:12] = 1001

IR[7:0] = 01110110



# More Register Annotation

R1 <- R2 + R3

R1 <- R2 + 0

R1 <- R1 and 0

R1 <- not R1

R1 <- R1 + 1

R1 <- R1 + R2

What do these do?

MDR <- MEM[MAR]


IR <- MDR

What do these do?

# Memory


- There is a need to use more than one number in a computer.
- Memory gives the ability to store and retrieve many numbers.
- Write to memory
  - Must provide the data to store.
  - Must provide the address to store it in.
  - Must tell the memory to write and not read.
- Reading from memory
  - Must provide the address to read.
  - Must tell the memory to read and not write.
- Think of it as multiple registers working together. All that is needed is a way to pick out the correct register and determine read or write.

# Memory Circuit

 


# Writing

- Write the number 5 to address 2.

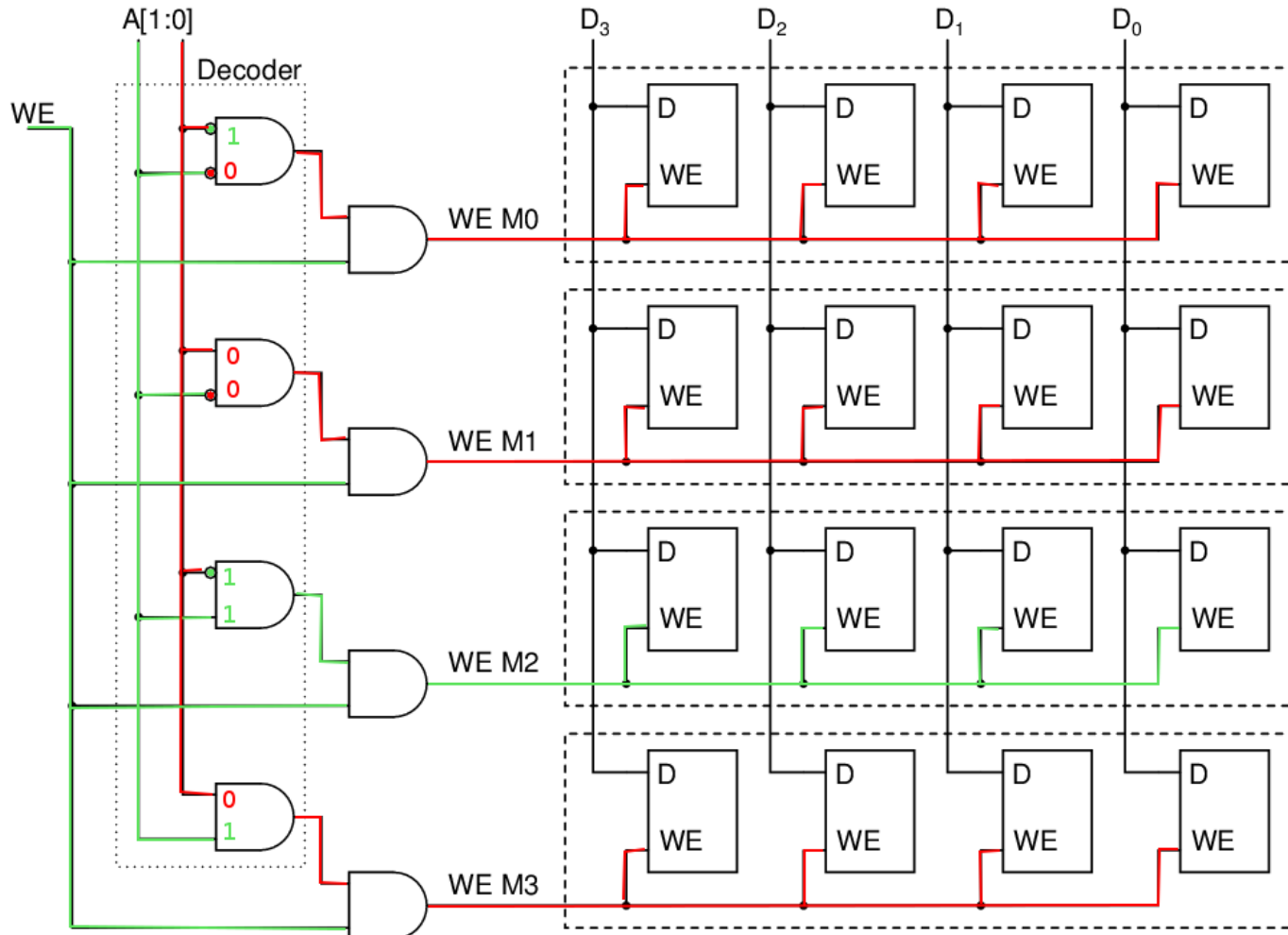


# 0101 Stored in Address 2

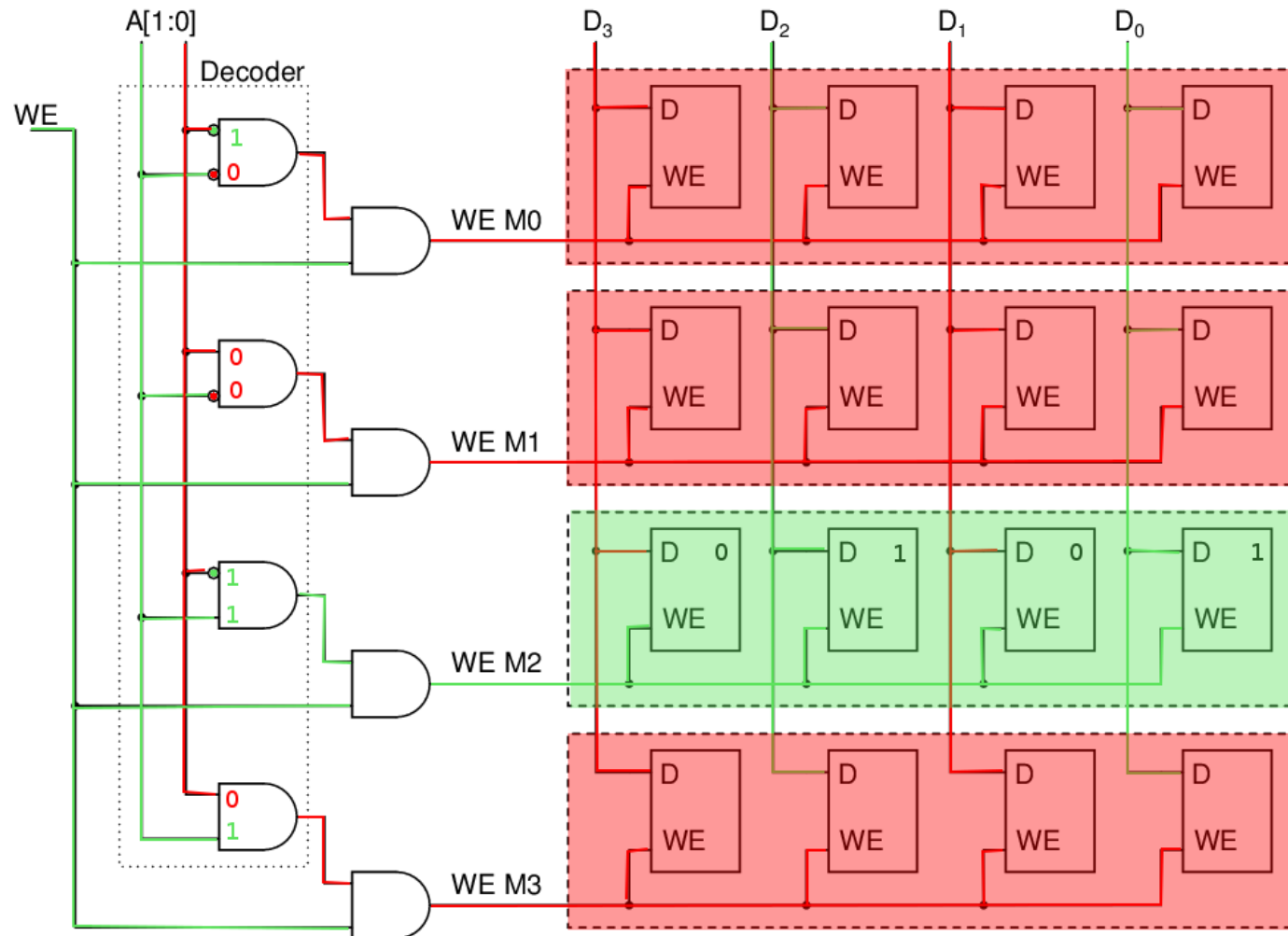


# Reading

- Read value stored in address 3

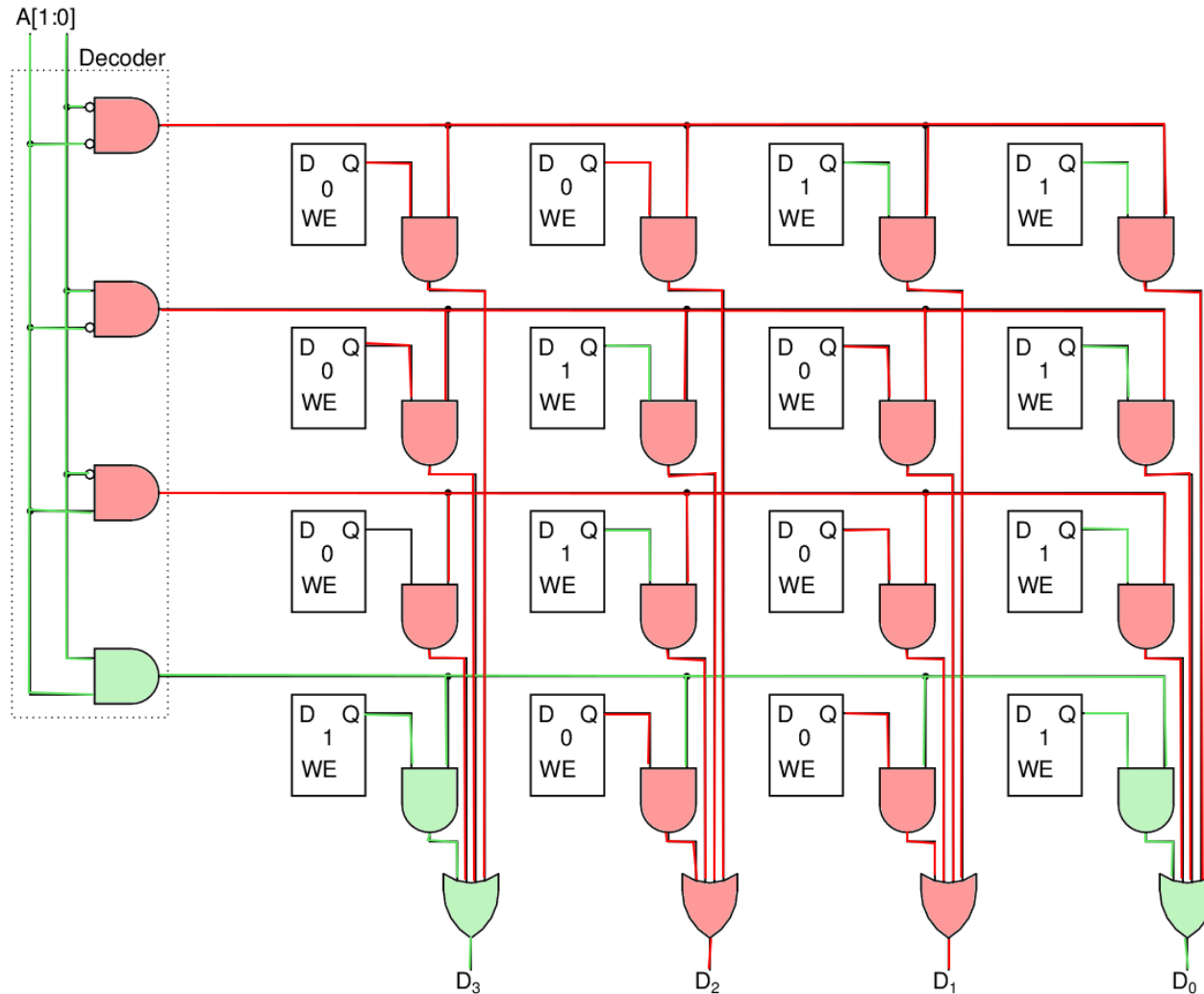


# Memory Circuit

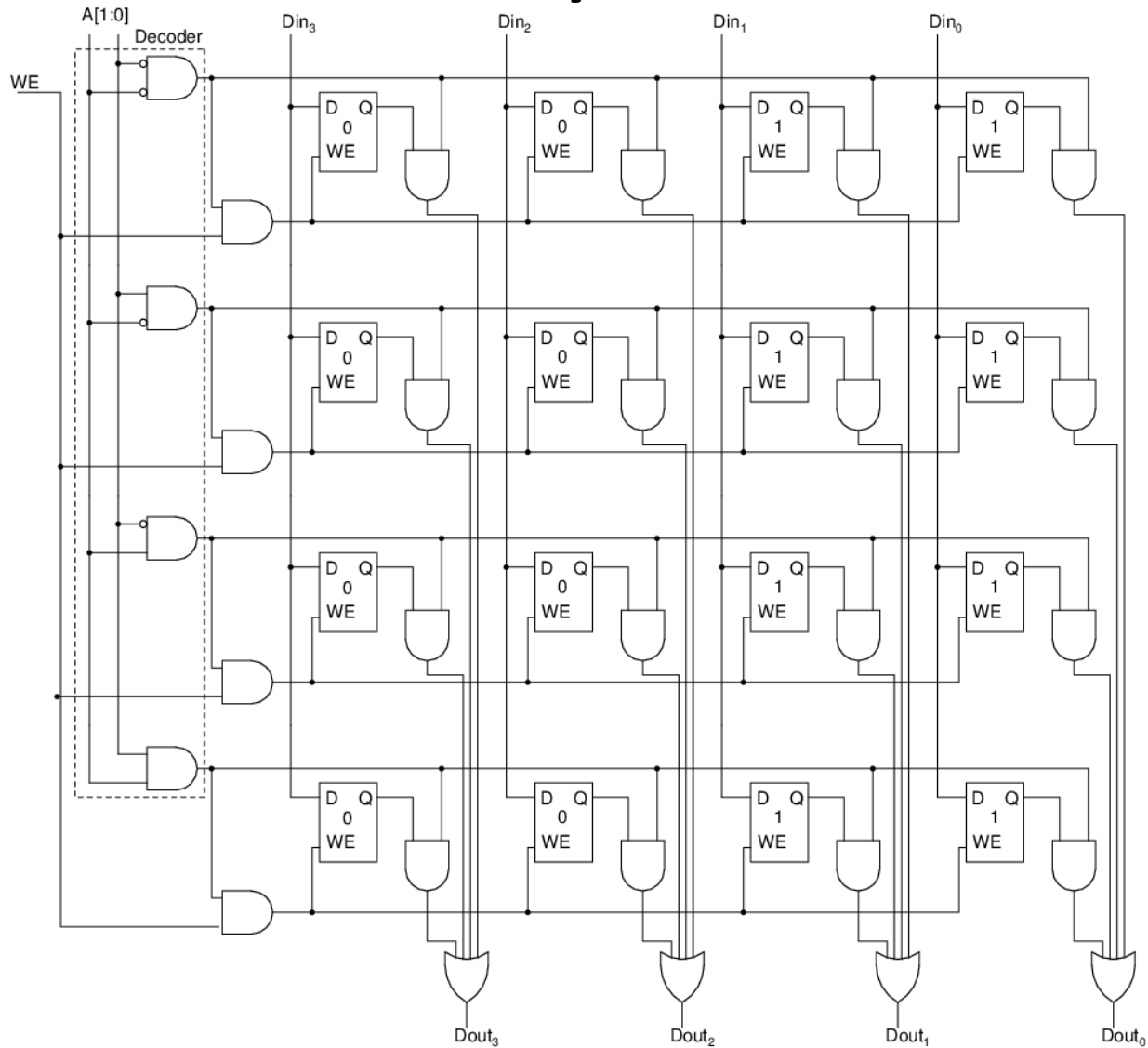

 
# Memory Block

- Addressability - How big are the data units?
- Address Space - How many data units are there?





# ALU

 


# Sequential Logic Circuits


- The circuits we studied before are called ***Combinational Logic***.
- ***Combinational Logic*** takes some inputs and determines the output by tracing the gate outputs from start to finish.
- ***Sequential Logic*** specifies an ordered sequence of outputs. For the sequence to be ordered the circuit must somehow "know" the last set of outputs.
- ***Sequential logic*** has memory units (latches) and those memory units provide input to determine the next sequence or state.

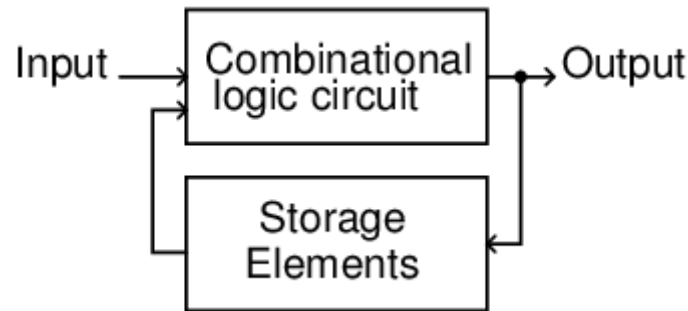
# Sequential Logic Block Diagram

Contains a combinational portion as well as some storage elements for keeping track of the current state.


 
# State Diagram

- Let's count from 0 to 3 in binary and repeat
  - 00 -> 01 -> 10 -> 11
- 
- This is a simple state diagram.



The states are specified by a labeled circle.  
The transitions are shown by the arrows.


# Finite State Machine

- A machine to generate all possible states and consists of:
  - a finite number of states
  - a finite number in external inputs
  - a finite number of external outputs
  - an explicit specification of all state transitions
  - an explicit specification of what determines an output


# State Diagram With Input

- Let's count from 0 to 3 in binary and repeat

- 00 -> 01 -> 10 -> 11

 


- This is a simple state diagram.

 

# Combination Lock Example

- Four states
  - A – Incorrect turns – lock not open
  - B – Correct first turn - lock not open
  - C – Correct second turn - lock not open
  - D – Correct third turn - lock open
- The combination is R13, L22, R3
- The internals of the lock represent the memory in the positioning of the opening mechanism.

# Combination Lock State Diagram

 


Are we done? Are all transitions labeled?


 
# Combination Lock State Diagram Complete

- We must show ALL transitions.
- This is much more complicated than before.




# Example 2 bit patterns

- 2 bits can form four states. They won't necessarily be in order.
- 1 switch input (0=count, 1=pause).
- Build a count up circuit with pause.
  - Draw the state diagram.
  - Create a truth table showing next states.
  - Build the circuit for each latch input


 
# State Diagram

- Each state must have a transition of 1 and a transition of 0 OUT of the state.
- Each state is a pair of D latches with the output connected to LEDs.
- State 00 represents a zero in both latches with both LEDs being off.
- State 11 represents a 1 in both latches with both LEDs being on.
- State 01 and 10 represent a zero in one latch and a zero in the other. One of the LEDs will be on. The other LED will be off.



 
 
# Latches and States Example 1

- $Q1=0$   $Q2=0$   $Sw=0$
- What do we need for proper state transition?



  
# Latches and States Example 2

- $Q1=1$   $Q2=0$   $Sw=1$
- What do we need on  $D1$  and  $D0$  for proper state transition?



# Count up with pause


| Current State |    |    | Next State |    |
|---------------|----|----|------------|----|
| Q1            | Q0 | Sw | D1         | D0 |
| 0             | 0  | 0  |            |    |
| 0             | 0  | 1  |            |    |
| 0             | 1  | 0  |            |    |
| 0             | 1  | 1  |            |    |
| 1             | 0  | 0  |            |    |
| 1             | 0  | 1  |            |    |
| 1             | 1  | 0  |            |    |
| 1             | 1  | 1  |            |    |

 

Q1 and Q0 are the current state.  
The switch SW represent the transition.


# Count up with pause

| Current State |    |    | Next State |    |
|---------------|----|----|------------|----|
| Q1            | Q0 | Sw | D1         | D0 |
| 0             | 0  | 0  | 0          | 1  |
| 0             | 0  | 1  |            |    |
| 0             | 1  | 0  |            |    |
| 0             | 1  | 1  |            |    |
| 1             | 0  | 0  |            |    |
| 1             | 0  | 1  |            |    |
| 1             | 1  | 0  |            |    |
| 1             | 1  | 1  |            |    |

 

# Count up with pause


| Current State |    |    | Next State |    |
|---------------|----|----|------------|----|
| Q1            | Q0 | Sw | D1         | D0 |
| 0             | 0  | 0  | 0          | 1  |
| 0             | 0  | 1  | 0          | 0  |
| 0             | 1  | 0  | 1          | 0  |
| 0             | 1  | 1  | 0          | 1  |
| 1             | 0  | 0  | 1          | 1  |
| 1             | 0  | 1  | 1          | 0  |
| 1             | 1  | 0  | 0          | 0  |
| 1             | 1  | 1  | 1          | 1  |

 




# Count up with pause


| Current State |           |           | Next State   |               |
|---------------|-----------|-----------|--------------|---------------|
| Q1<br>(A)     | Q0<br>(B) | Sw<br>(C) | D1<br>(Out1) | D0<br>(Out 2) |
| 0             | 0         | 0         | 0            | 1             |
| 0             | 0         | 1         | 0            | 0             |
| 0             | 1         | 0         | 1            | 0             |
| 0             | 1         | 1         | 0            | 1             |
| 1             | 0         | 0         | 1            | 1             |
| 1             | 0         | 1         | 1            | 0             |
| 1             | 1         | 0         | 0            | 0             |
| 1             | 1         | 1         | 1            | 1             |

 

# Count up with pause

| Current State |           |           | Next State   |               |
|---------------|-----------|-----------|--------------|---------------|
| Q1<br>(A)     | Q0<br>(B) | Sw<br>(C) | D1<br>(Out1) | D0<br>(Out 2) |
| 0             | 0         | 0         | 0            | 1             |
| 0             | 0         | 1         | 0            | 0             |
| 0             | 1         | 0         | 1            | 0             |
| 0             | 1         | 1         | 0            | 1             |
| 1             | 0         | 0         | 1            | 1             |
| 1             | 0         | 1         | 1            | 0             |
| 1             | 1         | 0         | 0            | 0             |
| 1             | 1         | 1         | 1            | 1             |

 

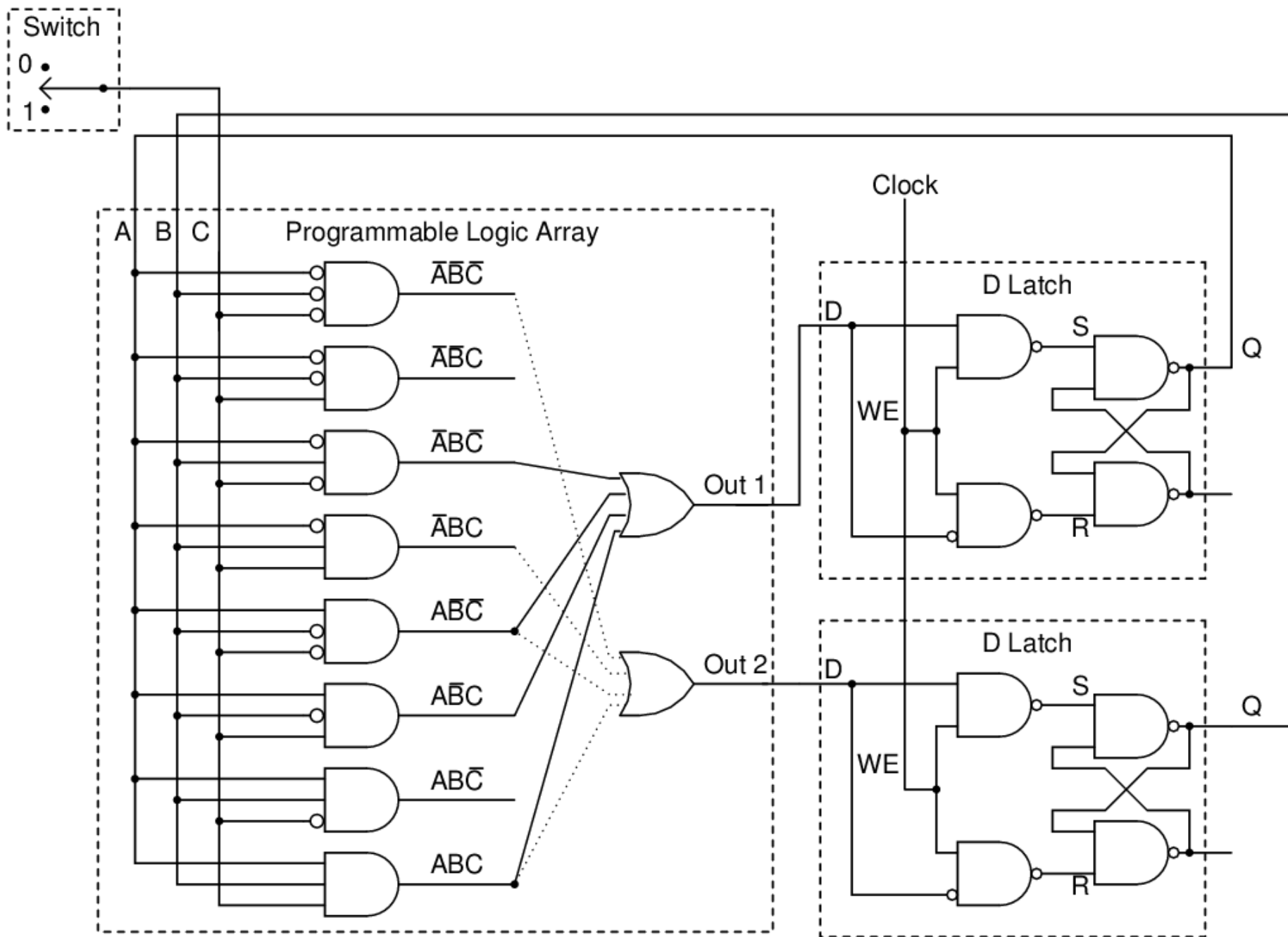

# Other Circuits

- Good test questions.
  - Count up and repeat  
00 - 01 - 10 - 11 - 00 - 01 - ...
  - Count up and stop at 11
  - Count down and repeat  
11 - 10 - 01 - 00 - 11 - 10 - ...
  - Count down and stop at 00
  - Both on – both off  
00 - 11 - 00 - 11 - ...
  - Alternate  
01 - 10 - 01 - 10 - ...
  - Pause, remain in current state.
  - others ...
- Could do any of the above on  $sw = 0$  and any other on  $sw = 1$

# Problem?

- There is a bit of a problem with using the D-Latch as shown with the clock.
- The output changes, which changes the inputs, which will change the output, etc.. as long as the clock is high.
- Use a master slave flip-flop to prevent the problem.

# Master – Slave Flip-flop

- First is set when clock goes high.
- Second is set from first when clock goes low.
- When clock is low, first cant be modified.

